


Applications Note:SY58203

Single Stage Flyback And PFC Regulator With Primary Side Control For LED Lighting Preliminary datasheet

General Description

The SY58203 is a single stage Flyback and PFC regulator targeting at LED lighting applications. It integrates a 700V MOSFET to decrease physical volume. It is a primary side controller without applying any secondary feedback circuit for low cost, and drives the Flyback converter in the quasi-resonant mode to achieve higher efficiency. It keeps the Flyback converter in constant on time operation to achieve high power factor.

Ordering Information

 

	Ordering Number	Package type	Note
I	SY58203FAC	SO8	

Features

- Integrated 700V MOSFET
- Primary side control eliminate to the opto-coupler.
- Valley turn-on of the primary MOSFET to achieve low switching losses
- 0.3V primary current sense reference voltage leads to a lower sense resistance thus a lower conduction loss.
- Low start up current: 15μA typical
- Reliable short LED and Open LED protection
- Power factor >0.90 with single-stage conversion.
- Maximum frequency limit: 120kHz
- Compact package: SO8

Applications

LED lighting

Recommended operating output power			
@I _{OUT} =300mA			
Products 90~264Vac			
SY58203 7W			

Typical Applications

 


Figure 1. Schematic Diagram SO8


 


Figure 2. Efficiency vs Input Voltage

 

Pinout (top view)



Top Mark: AGF xyz (device code: AGF, x=year code, y=week code, z= lot number code)

-			
	Pin Name	Pin number SO8	Pin Description
	GND	1	Ground pin
	Source	2	Source pin of the internal primary MOSFET. Connect the sense resistor to this Pin and the GND pin. (current sense resister R_S : $R_S = k \frac{V_{REF} \times N_{PS}}{I_{OUT}}$, $k = 0.167$)
	NC	3	(0
	Drain	4	Drain of the internal power MOSFET.
	NC	5	
	VIN	6	Power supply pin. This pin also provides output over voltage protection along with ZCS pin.
	COMP	7	Loop compensation pin. Connect a RC network across this pin and ground to stabilize the control loop.
	ZCS	8 411	Inductor current zero-crossing detection pin. This pin receives the auxiliary winding voltage by a resister divider and detects the inductor current zero crossing point. This pin also provides over voltage protection and line regulation modification function simultaneously. If the voltage on this pin is above $V_{ZCS,OVP}$, the IC would enter over voltage protection mode. Good line regulation can be achieved by adjusting the upper resistor of the divider.
silerd	Con	S.	





Absolute	Maximum	Ratings (Note 1)
----------	----------------	------------------

•	
VIN	
Supply current I _{VIN}	30mA
ZCS	
COMP,Source	
Drain	700V
Power Dissipation, @ TA = 25°C SO8	1.1W
Package Thermal Resistance (Note 2)	
SO8, θ JA	88°C/W
SO8, θ JC	45°C/W
Temperature Range	
Lead Temperature (Soldering, 10 sec.)	260°C
Storage Temperature Range	
Storage remperature runge	05 € 10 150 €

Recommended Operating Conditions (Note 3)

Block Diagram

 


Figure 3. Block Diagram



Electrical Characteristics

 $(V_{IN} = 12V \text{ (Note 3)}, T_A = 25^{\circ}\text{C unless otherwise specified)}$

Parameter	Symbol	Test Conditions	Min	Тур	Max	Unit
Power Supply Section	Symbol	Test conditions	IVIIII	Тур	IVIAX	Omt
Input voltage range	V_{VIN}		8		15.4	V
VIN turn-on threshold	VVIN		0		17.6	V
VIN turn-off threshold	V _{VIN,ON}		6.0		7.9	V
	V _{VIN,OFF}		0.0	V .0.95	7.9	V
VIN OVP voltage	V _{VIN,OVP}	37 37		$V_{VIN_ON} + 0.85$		
Start up Current	I _{ST}	V _{VIN} <v<sub>VIN,OFF</v<sub>		15		μA
Operating Current	I_{VIN}	$C_L=100pF, f=15kHz$		10		mA
Shunt current in OVP mode	$I_{VIN,OVP}$	$V_{VIN} > V_{VIN,OVP}$	1.6	2"	2.5	mA
Error Amplifier Section				<u>020</u>		
Internal reference voltage	V_{REF}		0.294	0.3	0.306	V
ZCS pin Section			$^{\prime}$			
ZCS pin OVP voltage	3.7		41	1.40	1.55	3.7
threshold	$V_{ZCS,OVP}$		1.41	1.48	1.55	V
Integrated MOSFET Section		, &O	•			
Breakdown Voltage	$V_{\rm BV}$	$V_{GS} = 0V, I_{DS} = 250 \mu A$	700			V
Current Sense Section(Source		ted MOSFET)				
Current limit reference	3.7			0.50		3.7
voltage	$V_{Source,MAX}$			0.50		V
PWM Section		10,7			•	
Max ON Time	T _{ON,MAX}	V _{COMP} =1.5V		24		μs
Min ON Time	T _{ON,MIN}	X		400		ns
Max OFF Time	T _{OFF,MAX}			39		μs
Min OFF Time	T _{OFF,MIN}	0		2		μs
Maximum switching				120		1.77
frequency	f_{MAX}			120		kHz
Thermal Section						
Thermal Shutdown				1.50		0.0
Temperature	${ m T_{SD}}$			150		°C
	1	<u> </u>	I.	l .	l .	1

Note 1: Stresses beyond the "Absolute Maximum Ratings" may cause permanent damage to the device. These are stress ratings only. Functional operation of the device at these or any other conditions beyond those indicated in the operational sections of the specification is not implied. Exposure to absolute maximum rating conditions for extended periods may affect device reliability.

Note 2: θ_{JA} is measured in the natural convection at $T_A = 25^{\circ}C$ on a low effective single layer thermal conductivity test board of JEDEC 51-3 thermal measurement standard. Test condition: Device mounted on 2" x 2" FR-4 substrate PCB, 2oz copper, with minimum recommended pad on top layer and thermal vias to bottom layer ground plane.

Note 3: Increase VIN pin voltage gradually higher than $V_{VIN,ON}$ voltage then turn down to 12V.



Operation

The SY58203 is a single stage Flyback and PFC regulator targeting at LED lighting applications.

It integrates a 700V MOSFET to decrease physical volume.

The device provides primary side control to eliminate the opto-couplers or the secondary feedback circuits, which would cut down the cost of the system.

High power factor is achieved by constant on operation mode, with which the control scheme and the circuit structure are both simple.

In order to reduce the switching losses and improve EMI performance, Quasi-Resonant switching mode is applied, which means to turn on the integrated MOSFET at voltage valley; the start up current of SY58203 is rather small (15 μ A typically) to reduce the standby power loss further; the maximum switching frequency is clamped to 120kHz to reduce switching losses and improve EMI performance when the converter is operated at light load condition.

SY58203 provides reliable protections such as Short Circuit Protection (SCP), Open LED Protection (OLP), Over Temperature Protection (OTP), etc.


SY58203 is available with SO8 package.

Application Information

Start up

After AC supply or DC BUS is powered on, the capacitor C_{VIN} across VIN and GND pin is charged up by BUS voltage through a start up resistor R_{ST} . Once V_{VIN} rises up to V_{VIN-ON} , the internal blocks start to work. V_{VIN} will be pulled down by internal consumption of IC until the auxiliary winding of Flyback transformer could supply enough energy to maintain V_{VIN} above $V_{VIN-OFF}$.

 The whole start up procedure is divided into two sections shown in Fig.4. t_{STC} is the C_{VIN} charged up section, and t_{STO} is the output voltage built-up section. The start up time t_{ST} composes of t_{STC} and t_{STO} , and usually t_{STO} is much smaller than t_{STC} .



The start up resistor R_{ST} and C_{VIN} are designed by rules below:

(a) Preset start-up resistor R_{ST} , make sure that the current through R_{ST} is larger than I_{ST} and smaller than I_{VIN_OVP}

$$\frac{V_{BUS}}{I_{VIN,OVP}} < R_{ST} < \frac{V_{BUS}}{I_{ST}} (1)$$

Where V_{BUS} is the BUS line voltage.

(b) Select C_{VIN} to obtain an ideal start up time t_{ST} , and ensure the output voltage is built up at one time.

$$C_{\text{VIN}} = \frac{(\frac{V_{\text{BUS}}}{R_{\text{ST}}} - I_{\text{ST}}) \times t_{\text{ST}}}{V_{\text{VIN,ON}}} (2)$$

(d) If the C_{VIN} is not big enough to build up the output voltage at one time. Increase C_{VIN} and decrease R_{ST} , go back to step (a) and redo such design flow until the ideal start up procedure is obtained.


Internal pre-charge design for quick start up

After V_{VIN} exceeds $V_{VIN,ON}$, V_{COMP} is pre-charged by an internal current source. The PWM block won't start to output PWM signals until V_{COMP} is over the initial voltage $V_{COMP,IC}$, which can be programmed by R_{COMP} . Such design is meant to reduce the start up time shown in Fig.5.

The voltage pre-charged $V_{\text{COMP_IC}}$ in start-up procedure can be programmed by R_{COMP}
 
$$V_{COMP\ IC} = 600 \text{mV} - 300 \mu \text{A} \times R_{COMP}$$
 (3)





 $Fig. 5 \ pre-charge \ scheme \ in \ start \ up \\ Where \ V_{COMP-IC} \ is \ the \ pre-charged \ voltage \ of \ COMP \ pin.$

Generally, a big capacitance of C_{COMP} is necessary to achieve high power factor and stabilize the system loop $(1\mu F\sim 2\mu F$ recommended); The voltage pre-charged in start-up procedure can be programmed by R_{COMP} ; On the other hand, larger R_{COMP} can provide larger phase margin for the control loop; A small ceramic capacitor is added to suppress high frequency interruption $(10pF\sim 100pF)$ is recommended if necessary)

Shut down

After AC supply or DC BUS is powered off, the energy stored in the BUS capacitor will be discharged. When the auxiliary winding of Flyback transformer can not supply enough energy to VIN pin, V_{VIN} will drop down. Once V_{VIN} is below $V_{\text{VIN-OFF}}$, the IC will stop working and V_{COMP} will be discharged to zero.

Primary-side constant-current control


Primary side control is applied to eliminate secondary feedback circuit or opto-coupler, which reduces the circuit cost. The switching waveforms are shown in Fig.6.

The output current I_{OUT} can be represented by,

$$I_{OUT} = \frac{I_{SP}}{2} \times \frac{t_{DIS}}{t_{S}} (4)$$

Where I_{SP} is the peak current of the secondary side; t_{DIS} is the discharge time of Flyback transformer; t_{S} is the switching period.

 The secondary peak current is related with primary peak current, if the effect of the leakage inductor is neglected.



$$I_{SP} = N_{PS} \times I_{PP} (5)$$

Where N_{PS} is the turns ratio of primary to secondary of the Flyback transformer.

Thus, I_{OUT} can be represented by

$$I_{OUT} = \frac{N_{PS} \times I_{PP}}{2} \times \frac{t_{DIS}}{t_s} (6)$$

The primary peak current I_{PP} and inductor current discharge time t_{DIS} can be detected by Source and ZCS pin, which is shown in Fig.7. These singular are processed and applied to the negative input of the gain modulator. In static state, the positive and negative inputs are equal.

$$V_{REF} = I_{PP} \times R_{S} \times \frac{t_{DIS}}{t_{S}} \times k_{1} (7)$$
Source
$$I_{PP} \times R_{S} \times \frac{t_{DIS}}{t_{S}} \times k_{1}$$

$$V_{REF}$$

$$V_{REF}$$

Fig.7 Output current detection diagram



Finally, the output current I_{OUT} can represented by

$$I_{OUT} = \frac{V_{REF} \times N_{PS}}{R_{S} \times 2 \times k_{1}} (8)$$

Where k_1 is the output current weight coefficient; V_{REF} is the internal reference voltage; R_S is the current sense resistor.

 $k_{\rm I},$ and V_{REF} are all internal constant parameters, I_{OUT} can be programmed by N_{PS} and $R_{S}.$


$$R_{s} = \frac{V_{REF} \times N_{PS}}{I_{OUT} \times 2 \times k_{1}} (9)$$

then

$$R_{S} = \frac{k \times V_{REF} \times N_{PS}}{I_{OUT}}, k = \frac{1}{2k_{1}} (10)$$

Quasi-Resonant Operation

 QR mode operation provides low turn-on switching losses for Flyback converter.



The voltage across drain and source of the primary integrated MOSFET is reflected by the auxiliary winding of the Flyback transformer. ZCS pin detects the voltage across the auxiliary winding by a resistor divider. When the voltage across drain and source of the primary integrated MOSFET is at voltage valley, the MOSFET would be turned on.

Over Voltage Protection (OVP) & Open LED Protection (OLP)

 


Fig.9 OVP&OLP

The output voltage is reflected by the auxiliary winding voltage of the Flyback transformer, and both ZCS pin and VIN pin provide over voltage protection function. When the load is null or large transient happens, the output voltage will exceed the rated value. When V_{VIN} exceeds $V_{\text{VIN,OVP}}$ or V_{ZCS} exceeds $V_{\text{ZCS,OVP}}$, the over voltage protection is triggered and the IC will discharge V_{VIN} by an internal current source $I_{\text{VIN,OVP}}$. Once V_{VIN} is below $V_{\text{VIN,OFF}}$, the IC will shut down and be charged again by BUS voltage through start up resistor. If the over voltage condition still exists, the system will operate in hiccup mode.

Thus, the turns of the auxiliary winding N_{AUX} and the resistor divider is related with the OVP function.

$$\frac{V_{ZCS_OVP}}{V_{OVP}} = \frac{N_{AUX}}{N_S} \times \frac{R_{ZCSD}}{R_{ZCSU} + R_{ZCSD}} (11)$$

$$\frac{V_{\text{VIN_OVP}}}{V_{\text{OVP}}} \ge \frac{N_{\text{AUX}}}{N_{\text{S}}} (12)$$

Where V_{OVP} is the output over voltage specification; R_{ZCSU} and R_{ZCSD} compose the resistor divider. The turns ratio of N_S to N_{AUX} and the ratio of R_{ZCSU} to R_{ZCSD} could be induced from equation (11) and (12).

Short Circuit Protection (SCP)

When the output is shorted to ground, the output voltage is clamped to zero. The voltage of the auxiliary winding is proportional to the output winding, so V_{VIN} will drop down without auxiliary winding supply. Once V_{VIN} is below $V_{VIN,OFF}$, the IC will shut down and be charged again by the BUS voltage through the start up resistor. If the short circuit condition still exists, the system will operate in hiccup mode.



SY58203

In order to guarantee SCP function not effected by voltage spike of auxiliary winding, a filter resistor R_{AUX} is needed (10 Ω typically) shown in Fig.9.

Line regulation modification

The IC provides line regulation modification function to improve line regulation performance.

Due to the sample delay of Source pin and other internal delay, the output current increases with increasing input BUS line voltage. A small compensation voltage $\Delta V_{\text{SE-C}}$ is added to Source pin during ON time to improve such performance. This $\Delta V_{\text{SE-C}}$ is adjusted by the upper resistor of the divider connected to ZCS pin.

$$\Delta V_{SE,C} = V_{BUS} \times \frac{N_{AUX}}{N_P} \times \frac{1}{R_{ZCSU}} \times k_2$$
(13)

Where R_{ZCSU} is the upper resistor of the divider; k_2 is an internal constant as the modification coefficient.

The compensation is mainly related with R_{ZCSU} , larger compensation is achieved with smaller R_{ZCSU} . Normally, R_{ZCS} ranges from $100k\Omega\sim1M\Omega$.

Then R_{ZCSD} can be selected by,

$$\frac{\frac{V_{ZCS_OVP}}{V_{OUT}} \times \frac{N_{s}}{N_{AUX}}}{1 - \frac{V_{ZCS_OVP}}{V_{OUT}} \times \frac{N_{s}}{N_{AUX}}} \times R_{ZCSU} > R_{ZCSD} (14),$$
And

$$R_{ZCSD} \ge \frac{\frac{V_{ZCS_OVP}}{V_{OVP}} \times \frac{N_S}{N_{AUX}}}{\frac{1}{V_{OVP}} \times \frac{N_S}{N_{AUX}}} \times R_{ZCSU} (15)$$

Where V_{OVP} is the output over voltage protection specification; V_{OUT} is the rated output voltage; R_{ZCSU} is the upper resistor of the divider; N_S and N_{AUX} are the turns of secondary winding and auxiliary winding separately.

Power design

A few applications are shown as below.

Products	Input range	Output current	Application	Temperature rise
	90Vac~264Vac	0.3A	5.0W/ER27	25°C
G1/50202	90Vac~264Vac	0.3A	5.5W/ER27	32°C
SY58203	90Vac~264Vac	0.3A	6.5W/ER27	38°C
	90Vac~264Vac	0.3A	7.0W/ER27	43°C

The test is operated in natural cooling condition at 25 °C ambient temperature.

Power Device Design

MOSFET and Diode

When the operation condition is with maximum input voltage and full load, the voltage stress of integrated MOSFET and secondary power diode is maximized;

$$V_{\text{MOS_DS_MAX}} = \sqrt{2} V_{\text{AC_MAX}} + N_{\text{PS}} \times (V_{\text{OUT}} + V_{\text{D_F}}) + \Delta V_{\text{S}} (16)$$

$$V_{\text{D_R_MAX}} = \frac{\sqrt{2} V_{\text{AC_MAX}}}{N_{\text{PS}}} + V_{\text{OUT}} (17)$$

Where $V_{AC,MAX}$ is maximum input AC RMS voltage; N_{PS} is the turns ratio of the Flyback transformer; V_{OUT} is the rated output voltage; $V_{D,F}$ is the forward voltage of secondary power diode; ΔV_S is the overshoot voltage clamped by RCD snubber during OFF time.

When the operation condition is with minimum input voltage and full load, the current stress of integrated MOSFET and power diode is maximized.

$$\begin{split} &I_{\text{MOS_PK_MAX}} \!=\! I_{\text{P_PK_MAX}} \left(18\right) \\ &I_{\text{MOS_RMS_MAX}} \!=\! I_{\text{P_RMS_MAX}} \left(19\right) \\ &I_{\text{D_PK_MAX}} \!=\! N_{\text{PS}} \!\times\! I_{\text{P_PK_MAX}} \left(20\right) \\ &I_{\text{D_AVG}} \!=\! I_{\text{OUT}} \left(21\right) \end{split}$$

Where $I_{P\text{-PK-MAX}}$ and $I_{P\text{-RMS-MAX}}$ are maximum primary peak current and RMS current, which will be introduced later.

Transformer (NPS and LM)

 N_{PS} is limited by the electrical stress of the internal power MOSFET:



$$N_{PS} \le \frac{V_{MOS_(BR)DS} \times 80\% - \sqrt{2}V_{AC_MAX} - \Delta V_{S}}{V_{OUT} + V_{D_F}}$$
 (22)

Where $V_{\text{MOS,(BR)DS}}$ is the breakdown voltage of the integrated MOSFET.

In Quasi-Resonant mode, each switching period cycle ts consists of three parts: current rising time t₁, current falling time t₂ and quasi-resonant time t₃ shown in Fig. 10.

 


Fig.10 switching waveforms

The system operates in the constant on time mode to achieve high power factor. The ON time increases with the input AO RMS voltage decreasing and the load increasing.) When the operation condition is with minimum input AC RMS voltage and full load, the ON time is maximized. On the other hand, when the input voltage is at the peak value, the OFF time is maximized. Thus, the minimum switching frequency f_{S-MIN} happens at the peak value of input voltage with minimum input AC RMS voltage and maximum load condition; Meanwhile, the maximum peak current through integrated MOSFET and the transformer happens.

Once the minimum frequency f_{S-MIN} is set, the inductance of the transformer could be induced. The design flow is shown as below:

$$N_{PS} \le \frac{V_{MOS_(BR)DS} \times 80\% - \sqrt{2}V_{AC_MAX} - \Delta V_{S}}{V_{OUT} + V_{D.F}}$$
 (23)

- **(b)** Preset minimum frequency f_{S-MIN}
- (c) Compute relative t_s , t_1 (t_3 is omitted to simplify the design here)

$$t_{s} = \frac{1}{f_{s_MIN}} (24)$$

$$t_{1} = \frac{t_{s} \times N_{PS} \times (V_{OUT} + V_{D_F})}{\sqrt{2}V_{AC_MIN} + N_{PS} \times (V_{OUT} + V_{D_F})} (25)$$

$$\begin{array}{l} \textbf{(d) Design inductance } L_{M} \\ L_{M} = \frac{V_{AC_MIN}^{2} \times t_{1}^{2} \times \eta}{2P_{OUT} \times t_{S}} \ (26) \end{array}$$

(e) Compute t₃

$$t_3 = \pi \times \sqrt{L_M \times C_{Drain}}$$
 (27)

Where C_{Drain} is the parasitic capacitance at drain of integrated MOSFET.

(f) Compute primary maximum peak current I_{P-PK-MAX} and RMS current I_{P-RMS-MAX} for the transformer

$$\begin{split} I_{P_{PK_MAX}} &= \frac{2P_{OUT} \times [\frac{L_{M}}{\sqrt{2}V_{AC_MIN}} + \frac{L_{M}}{N_{PS} \times (V_{OUT} + V_{D_F})}]}{L_{M} \times \eta} \\ &+ \frac{\sqrt{4P_{OUT}^{2} \times [\frac{L_{M}}{\sqrt{2}V_{AC_MIN}} + \frac{L_{M}}{N_{PS} \times (V_{OUT} + V_{D_F})}]^{2} + 4L_{M} \times \eta \times P_{OUT} \times t_{3}}}{L_{M} \times \eta} \end{split}$$

Where η is the efficiency; P_{OUT} is rated full load power

Adjust t1 and tS to t1' and tS' considering the effect of t3 $t_{s}^{\prime} = \frac{\eta \times L_{M} \times I_{P_PK_MAX}^{2}}{4P_{OUT}} (29)$

$$t_{1}' = \frac{L_{M} \times I_{P_PK_MAX}}{\sqrt{2} V_{AC_MIN}} (30)$$

$$I_{P_RMS_MAX} \approx \sqrt{\frac{t_{1}'}{6t_{c}'}} \times I_{P_PK_MAX} (31)$$





(g) Compute secondary maximum peak current $I_{S\text{-PK-MAX}}$ and RMS current $I_{S\text{-RMS-MAX}}$ for the transformer fabrication.

$$I_{S_PK_MAX} = N_{PS} \times I_{P_PK_MAX} (32)$$

$$t_{2}^{'}=t_{S}^{'}-t_{1}^{'}-t_{3}(33)$$

$$I_{S_RMS_MAX} \approx \sqrt{\frac{t_{2}^{'}}{6t_{S}^{'}}} \times I_{S_PK_MAX}(34)$$

(h) Make sure that t_1 ', t_2 ', t_3 ' are not out of the range given in EC table.

Transformer design (NP,NS,NAUX)

The design of the transformer is similar with ordinary Flyback transformer, the parameters below are necessary:

Necessary parameters				
Turns ratio	N_{PS}			
Inductance	L_{M}			
Primary maximum current	I _{P-PK-MAX}			
Primary maximum RMS current	I _{P-RMS-MAX}			
Secondary maximum RMS current	$I_{S-RMS-MAX}$			

The design rules are as followed:

- (a) Select the magnetic core style, identify the effective area $A_{\rm e.}$
- (b) Preset the maximum magnetic flux ΔB

 $\Delta B = 0.22 \sim 0.26 T$

(c) Compute primary turn N_F

$$N_{p} = \frac{I_{M} \times I_{P_PK_MAX}}{\Delta B \times A_{e}} (35)$$

(d) Compute secondary turn N_S

$$N_{\rm S} = \frac{N_{\rm P}}{N_{\rm PS}} (36)$$

(e) compute auxiliary turn N_{AUX}

$$N_{AUX} = N_S \times \frac{V_{VIN}}{V_{OUT}} (37)$$

Where V_{VIN} is the working voltage of VIN pin (10V~11V is recommended).

(f) Select an appropriate wire diameter

With I_{P-RMS-MAX} and I_{S-RMS-MAX}, select appropriate wire to make sure the current density ranges from 4A/mm² to 10A/mm²

(g) If the winding area of the core and bobbin is not enough, reselect the core style, go to (a) and redesign the transformer until the ideal transformer is achieved.

Output capacitor Cout

Preset the output current ripple ΔI_{OUT} , C_{OUT} is induced by

$$C_{\text{OUT}} = \frac{\sqrt{(\frac{2I_{\text{OUT}}}{\Delta I_{\text{OUT}}})^2 - 1}}{4\pi f_{\text{AC}} R_{\text{LED}}} (38)$$

Where I_{OUT} is the rated output current; ΔI_{OUT} is the demanded current ripple; f_{AC} is the input AC supply frequency; R_{LED} is the equivalent series resistor of the LED load.

RCD snubber for MOSFET

The power loss of the snubber P_{RCD} is evaluated first

$$P_{\text{RCD}} = \frac{N_{\text{PS}} \times (V_{\text{OUT}} + V_{\text{D_F}}) + \Delta V_{\text{S}}}{\Delta V_{\text{S}}} \times \frac{L_{\text{K}}}{L_{\text{M}}} \times P_{\text{OUT}}$$
(39)

Where N_{PS} is the turns ratio of the Flyback transformer; V_{OUT} is the output voltage; $V_{D\text{-}F}$ is the forward voltage of the power diode; ΔV_S is the overshoot voltage clamped by RCD snubber; L_K is the leakage inductor; L_M is the inductance of the Flyback transformer; P_{OUT} is the output power.

The R_{RCD} is related with the power loss:

$$R_{RCD} = \frac{(N_{PS} \times (V_{OUT} + V_{D_F}) + \Delta V_S)^2}{P_{RCD}} (40)$$

The C_{RCD} is related with the voltage ripple of the snubber $\Delta V_{\text{C-RCD}}$:

$$C_{RCD} = \frac{N_{PS} \times (V_{OUT} + V_{D_F}) + \Delta V_{S}}{R_{RCD} f_{S} \Delta V_{CRCD}}$$
(41)





Layout

- (a) To achieve better EMI performance and reduce line frequency ripples, the output of the bridge rectifier should be connected to the BUS line capacitor first, then to the switching circuit.
- (b) The circuit loop of all switching circuit should be kept small: primary power loop, secondary loop and auxiliary power loop.
- (c) The connection of primary ground is recommended as:

Ground ①: ground of BUS line capacitor

Ground ②: ground of bias supply capacitor


Ground ③: ground node of auxiliary winding

Ground 4: ground of signal trace

Ground ⑤: primary ground node of Y capacitor

Ground 6: ground node of current sample resistor.

 - (d) bias supply trace should be connected to the bias supply capacitor first instead of GND pin. The bias supply capacitor should be put beside the IC.
- (e) Loop of 'Source pin current sample resistor GND pin' should be kept as small as possible.
- (f) The resistor divider connected to ZCS pin is recommended to be put beside the IC.





Design Example

A design example of typical application is shown below step by step.

#1. Identify design specification

Design Specification				~
V _{AC} (RMS)	90V~264V	V_{OUT}	24V	70
I_{OUT}	330mA	η	85%	

#2. Transformer design (N_{PS}, L_{M})

Refer to Power Device Design

Conditions			
$V_{AC,MIN}$	90V	V_{AC-MAX}	264V
$\triangle V_{S}$	50V	V _{MOS-(BR)DS}	700V
P _{OUT}	8W	$V_{\mathrm{D,F}}$	1V
C_{Drain}	100pF	f_{S-MIN}	65kHz

(a)Compute turns ratio N_{PS} first

$$\begin{split} N_{PS} &\leq \frac{V_{MOS_(BR)DS} \times 80\% - \sqrt{2}V_{AC_MAX} - \Delta V_{S}}{V_{OUT} + V_{D,F}} \\ &= \frac{700V \times 0.8 - \sqrt{2} \times 264V - 50V}{24V + 1V} \\ &= 5.48 \end{split}$$

N_{PS} is set to

$$N_{PS} = 4.5$$

(b)f_{S,MIN} is preset

$$f_{S_{-MIN}} = 65kHz$$

(c) Compute the switching period t_S and ON time t_1 at the peak of input voltage.

$$t_{s} = \frac{1}{f_{s \text{ MIN}}} = 15.3 \mu s$$

$$t_{1} = \frac{t_{s} \times N_{PS} \times (V_{OUT} + V_{D_{_F}})}{\sqrt{2}V_{AC_MIN} + N_{PS} \times (V_{OUT} + V_{D_{_F}})}$$

$$= \frac{15.3\mu s \times 4.5 \times (24V + 1V)}{\sqrt{2} \times 90V + 4.5 \times (24V + 1V)}$$

$$= 7.2\mu s$$





(d) Compute the inductance L_M

$$\begin{split} L_{M} &= \frac{V_{AC_MIN}^{2} \times t_{1}^{2} \times \eta}{2P_{OUT} \times t_{s}} \\ &= \frac{90V^{2} \times 7.2\mu s^{2} \times 0.85}{2 \times 8W \times 15.3\mu s} \\ &= 1.46mH \end{split}$$

Set

$$L_{\rm M}=1.4{\rm mH}$$

(e) Compute the quasi-resonant time t₃

$$t_3 = \pi \times \sqrt{L_M \times C_{Drain}}$$

= $\pi \times \sqrt{1.4 \text{mH} \times 100 \text{pF}}$
= $1.2 \mu \text{s}$

(f) Compute primary maximum peak current $I_{P-PK-MAX}$

Set
$$L_{M}=1.4\text{mH}$$
(e) Compute the quasi-resonant time t_{3}

$$t_{3}=\pi\times\sqrt{L_{M}\times C_{Drain}}$$

$$=\pi\times\sqrt{1.4\text{mH}\times 100\text{pF}}$$

$$=1.2\mu\text{s}$$
(f) Compute primary maximum peak current $I_{P-PK-MAX}$

$$I_{P-PK-MAX}=\frac{2P_{\text{OUT}}\times[\frac{L_{M}}{\sqrt{2}V_{\text{AC}-MIN}}+\frac{L_{M}}{N_{PS}\times(V_{\text{OUT}}+V_{D,F})}]}{L_{M}\times\eta}$$

$$+\frac{\sqrt{4P_{\text{OUT}}^{2}\times[\frac{L_{M}}{\sqrt{2}V_{\text{AC}-MIN}}+\frac{L_{M}}{N_{PS}\times(V_{\text{OUT}}+V_{D,F})}]^{2}+4L_{M}\times\eta\times P_{\text{OUT}}\times t_{3}}}{L_{M}\times\eta}$$

$$=0.685\text{A}$$

Adjust switching period t_S and QN time t_1 to t_S' and t_1' .

$$t_{s}' = \frac{\eta \times L_{M} \times I_{P_PK_MAX}^{2}}{4P_{OUT}}$$

$$= \frac{0.85 \times 1.4 \text{mH} \times 0.685 \text{A}^{2}}{4 \times 8 \text{W}}$$

$$= 17.4 \text{ µs}$$

$$t = \frac{L_{M} \times I_{P_PK_MAX}}{\sqrt{2} V_{\text{AC_MIN}}}$$

$$= \frac{1.4 \text{mH} \times 0.69 \text{A}}{\sqrt{2} V_{\text{AC_MIN}}}$$

Compute primary maximum RMS current $I_{P\text{-RMS-MAX}}$

$$I_{P_RMS_MAX} \approx \sqrt{\frac{t_1'}{6t_S'}} \times I_{P_PK_MAX} = \sqrt{\frac{7.59\mu s}{6 \times 17.4\mu s}} \times 0.685 A = 0.185 A$$



(g) Compute secondary maximum peak current and the maximum RMS current.

$$I_{S_PK_MAX} = N_{PS} \times I_{P_PK_MAX} = 4.5 \times 0.685 A = 3.08 A$$

$$t_2 = t_3 - t_1 - t_3 = 17.4 \mu s - 7.59 \mu s - 1.2 \mu s = 8.6 \mu s$$

$$I_{S,RMS,MAX} \approx \sqrt{\frac{t_2'}{6t_S'}} \times I_{S_PK_MAX} = \sqrt{\frac{8.6\mu s}{6 \times 17.4\mu s}} \times 3.08A = 0.88A$$

- #3. Select secondary power diode
- (a) Compute the voltage and the current stress of secondary power diode

$$V_{D_{_R_MAX}} = \frac{\sqrt{2}V_{AC_MAX}}{N_{PS}} + V_{OUT} = \frac{\sqrt{2} \times 264V}{4.5} + 25V = 108V$$

$$I_{D_PK_MAX}\!=\!\!N_{PS}\!\times\!I_{P_PK_MAX}\!=\!\!4.5\!\times\!0.685A\!=\!3.08A$$

$$I_{D \text{ AVG}} = I_{OUT} = 0.33 A$$

$I_{S,RMS,MAX} \approx \sqrt{\frac{t_2'}{6t_S'}} \times I_{S_PK_MAX} = \sqrt{\frac{8.6\mu s}{6 \times 17.4\mu s}} \times 3.08A = 0.88A$
#3. Select secondary power diode
(a) Compute the voltage and the current stress of secondary power diode
$I_{S,RMS,MAX} \approx \sqrt{\frac{t_2'}{6t_S'}} \times I_{S,PK,MAX} = \sqrt{\frac{8.6 \mu s}{6 \times 17.4 \mu s}} \times 3.08 A = 0.88 A$ #3. Select secondary power diode (a) Compute the voltage and the current stress of secondary power diode $V_{D,R,MAX} = \frac{\sqrt{2} V_{AC,MAX}}{N_{PS}} + V_{OUT} = \frac{\sqrt{2} \times 264 V}{4.5} + 25 V = 108 V$ $I_{D,PK,MAX} = N_{PS} \times I_{P,PK,MAX} = 4.5 \times 0.685 A = 3.08 A$ $I_{D,AVG} = I_{OUT} = 0.33 A$ #4. Select the output capacitor C_{OUT}
$I_{D_{PK_MAX}} = N_{PS} \times I_{P_{PK_MAX}} = 4.5 \times 0.685 A = 3.08A$
$I_{D_{AVG}} = I_{OUT} = 0.33A$
#4. Select the output capacitor C _{OUT}
Refer to Power Device Design
Conditions
I_{OUT} 330mA ΔI_{OUT} 0.3 I_{OUT}
f_{AC} 50Hz R_{LED} $8 \times 1.6 \Omega$

The output capacitor is

$$C_{OUT} = \frac{\sqrt{(\frac{2I_{OUT}}{\Delta I_{OUT}})^2 - 1}}{4\pi f_{AC}R_{DED}} = \frac{\sqrt{(\frac{2 \times 0.33A}{0.3 \times 0.33A})^2 - 1}}{4\pi \times 50Hz \times 8 \times 1.6\Omega} = 820\mu F$$

#5. Design RCD snubber

Refer to Power Device Design

Conditions					
V _{OUT}	24V	ΔV_{S}	50V		
N_{PS}	4.5	L_{K}/L_{M}	1%		
P _{OUT}	8W				

The power loss of the snubber is

$$P_{\text{RCD}} = \frac{N_{\text{PS}} \times (V_{\text{OUT}} + V_{\text{D_F}}) + \Delta V_{\text{S}}}{\Delta V_{\text{S}}} \times \frac{L_{\text{K}}}{L_{\text{M}}} \times P_{\text{OUT}} = \frac{4.5 \times (24 \text{V} + 1 \text{V}) + 50 \text{V}}{50 \text{V}} \times 0.01 \times 8 \text{W} = 0.26 \text{W}$$



The resistor of the snubber is

$$R_{_{RCD}} = \frac{(N_{_{PS}} \times (V_{_{OUT}} + V_{_{D,F}}) + \Delta V_{_{S}})^2}{P_{_{RCD}}} = \frac{(4.5 \times (24V + 1V) + 50V)^2}{0.26W} = 101k\Omega$$

The capacitor of the snubber is

$$C_{\text{RCD}} = \frac{N_{\text{PS}} \times (V_{\text{OUT}} + V_{\text{D_F}}) + \Delta V_{\text{S}}}{R_{\text{RCD}} f_{\text{S}} \Delta V_{\text{C_RCD}}} = \frac{4.5 \times (24 \text{V} + 1 \text{V}) + 50 \text{V}}{101 \text{k} \Omega \times 100 \text{kHz} \times 25 \text{V}} = 0.64 \text{nF}$$

#6. Set VIN pin

Refer to Start up

Conditions			, <u>~</u> 0.
$V_{BUS-MIN}$	90V×1.414	$V_{BUS-MAX}$	264V×1.414
I_{ST}	15μA (typical)	V _{IN-ON}	16V (typical)
I _{VIN-OVP}	2mA (typical)	t_{ST}	500ms (designed by user)

$$R_{ST} < \frac{V_{BUS}}{I_{ST}} = \frac{90V \times 1.414}{15\mu A} = 8.48M\Omega$$

$$R_{st} = 470 k\Omega \times 2 = 940 k\Omega$$

(b) Design C_{VIN}

$$C_{VIN} = \frac{(\frac{V_{BUS}}{R_{ST}} I_{ST}) \times t_{ST}}{V_{VIN_ON}} = \frac{(\frac{90V \times 1.414}{750k\Omega} - 15\mu A) \times 500ms}{16V} = 4.83\mu F$$

#7 Set COMP pin

Refer to Internal pre-charge design for quick start up

Parameters designed			
R _{COMP}	500Ω	$V_{COMP,IC}$	450mV
C_{COMP1}	2μF	C_{COMP2}	100pF



#8 Set current sense resistor to achieve ideal output current

Refer to Primary-side constant-current control

Known conditions at this step			
k	0.167	N_{PS}	4.5
V_{REF}	0.3V	I_{OUT}	0.33A

The current sense resistor is

$$R_{S} = \frac{k \times V_{REF} \times N_{PS}}{I_{OUT}} = \frac{0.167 \times 0.3V \times 4.5}{0.33A} = 0.65\Omega$$

#9 set ZCS pin

Refer to Line regulation modification and Over Voltage Protection (OVP) & Open Loop Protection (OLP)

First identify R_{ZCSU} need for line regulation.

Known conditions at this	s step	0	
k_2	68		
Parameters Designed		0,0,	
R _{ZCSU}	150kΩ		

Then compute R_{7CSD}

Then compute RZCSD			
Conditions			
V _{ZCS_OVP}	1.42V	V _{OVP}	30V
V _{OUT}	24V		
Parameters designed	101		
R _{ZCSU}	150kΩ		
N _S / N _{AUX}	2.4		

$$R_{ZCSD} < \frac{\frac{V_{ZCS_OVP}}{V_{OUT}} \times \frac{N_S}{N_{AUX}}}{1 - \frac{V_{ZCS_OVP}}{V_{OUT}} \times \frac{N_S}{N_{AUX}}} \times R_{ZCSU} = \frac{\frac{1.42V}{24V} \times 2.4}{1 - \frac{1.42V}{24V} \times 2.4} \times 150k\Omega = 24.8k\Omega$$


$$R_{ZOSD} \ge \frac{\frac{V_{ZCS_OVP}}{V_{OVP}} \times \frac{N_{S}}{N_{AUX}}}{1 - \frac{V_{ZCS_OVP}}{V_{OVP}} \times \frac{N_{S}}{N_{AUX}}} \times R_{ZCSU} = \frac{\frac{1.42V}{30V} \times 2.4}{1 - \frac{1.42V}{30V} \times 2.4} \times 150k\Omega = 19.2k\Omega$$

 R_{ZCSD} is set to

 R_{zcsd} =22.1k Ω




#10 Final result

 



SO8 Package Outline & PCB Layout Design

 

Notes: All dimensions are in millimeters.

All dimensions don't include mold flash & metal burr.